


## Circuits Practice

$$V = IR$$

$$R_{eq} = R_1 + R_2 + \dots$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$


1)

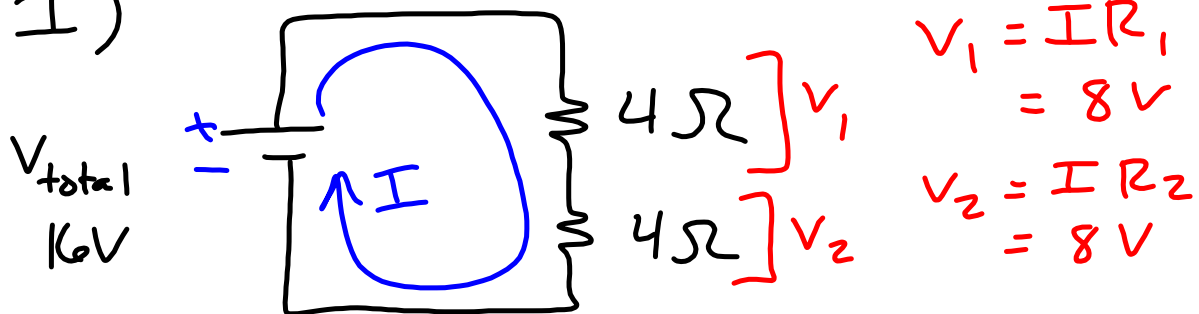

conventional current goes from + to -

$$R_{eq} = 4\Omega + 4\Omega = 8\Omega$$
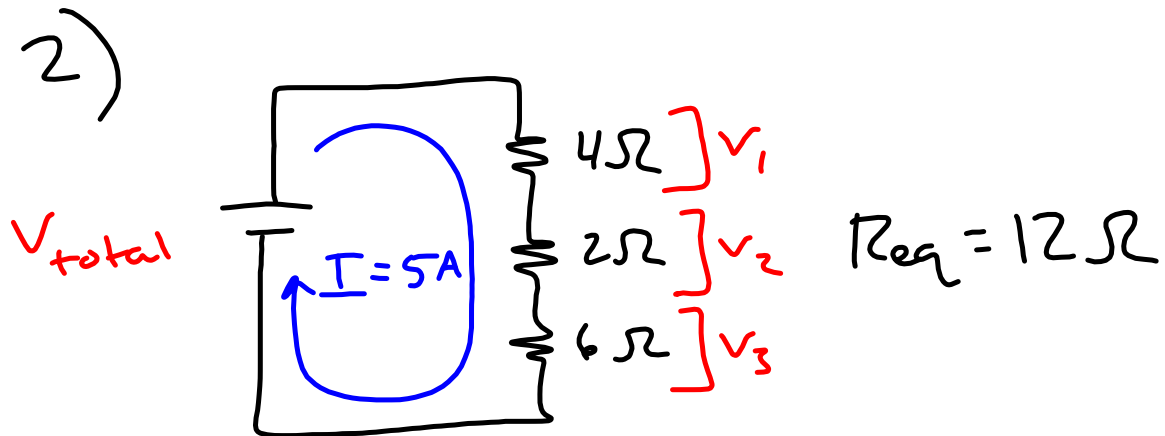
$$I = \frac{V_{total}}{R_{eq}} = \frac{16V}{8\Omega} = 2A$$




$$V_{total} = I R_{eq} = (5A)(12\Omega) = 60V$$

$$V_1 = I R_1 = 20V$$

$$V_2 = I R_2 = 10V$$

$$V_3 = I R_3 = 30V$$

3)

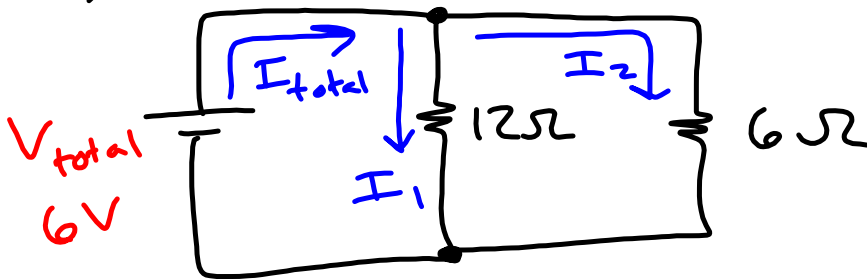

$$I_1 = \frac{V_{total}}{R_1} = 0.5 A$$

$$I_2 = \frac{V_{total}}{R_2} = \frac{6V}{6\Omega} = 1 A$$

$$I_{total} = I_1 + I_2 = 1.5 A$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\begin{aligned} \frac{1}{R_{eq}} &= \frac{1}{12\Omega} + \frac{1}{6\Omega} \\ &= \frac{3}{12\Omega} = \frac{1}{4\Omega} \end{aligned}$$

$$R_{eq} = 4\Omega$$

$$R_{eq} = 4\Omega$$